

Homework (Due Tuesday October 23 at 3PM).

Do either (1) or (2) below

- (1) Write a one page essay on the contributions of either
(a) **Charles-Augustin de Coulomb**, or (b) **Georg Ohm**.
(1 page 12 pt font single spaced)

- (2) Solve the circuit below by finding the current (amperes) for an 18 volt fuel source if each resistance is 6 ohms.

