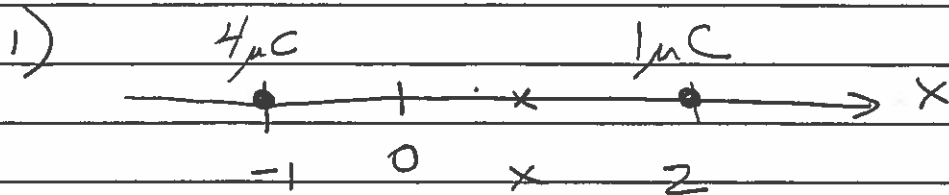


# Test 1 SF7 Phy 2005

## Solutions

①



region I

II

III

In regions I and III, any test charge will experience a nonzero force because the field from both charges will point in same direction, i.e. can't cancel. So put the test charge in region II.  $\vec{E} = 0$  is

$$F_{\text{net}} = E_4 + E_1 = kQ_4 \frac{1}{(x+1)^2} - kQ_1 \frac{1}{(2-x)^2} = 0$$

$$Q_4 = 4 \mu\text{C}; Q_1 = 1 \mu\text{C}$$

$$4(2-x)^2 = (x+1)^2 \Rightarrow 2(2-x) = \pm(x+1)$$

2 solns:

$$\text{i) } 2(2-x) = x+1 \Rightarrow x=1 \quad \checkmark$$

$$\text{ii) } 2(2-x) = -x-1 \Rightarrow x=5 \quad \times$$




(outside region II)

$\Rightarrow x=1$  is correct


$$2) \text{ Current} = \frac{\Delta Q}{\Delta t} = \frac{\text{charge}}{\text{time}}$$

$$\frac{\Delta Q}{60\text{s}} = 6 \text{ Amp} \Rightarrow \Delta Q = 360 \text{ C}$$

3)

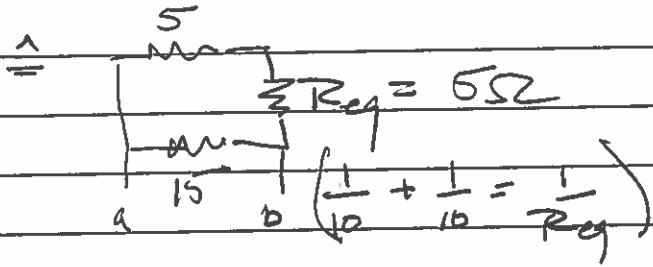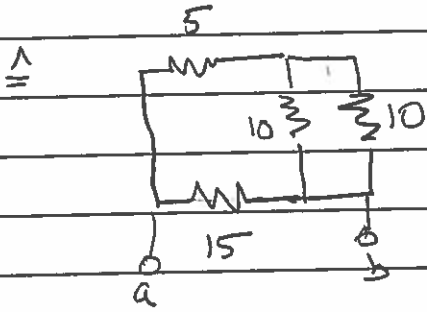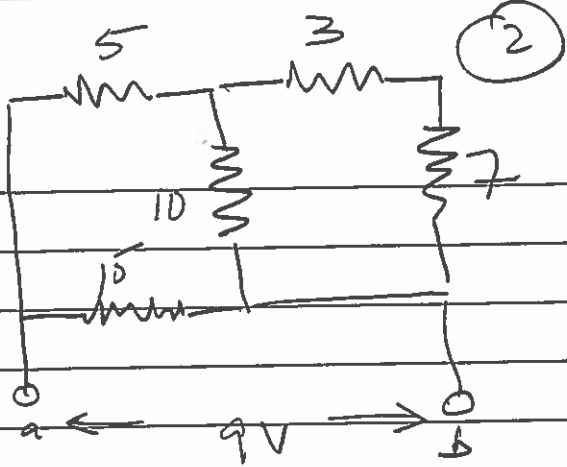


$$10 = 5 + 5$$

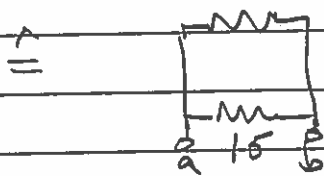


$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{15} = \frac{5}{30}$$

$$R_{eq}' = 6\Omega$$

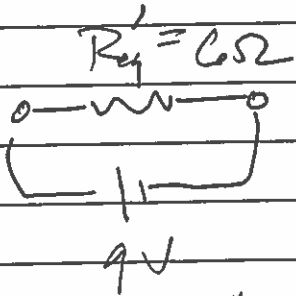

$$\Rightarrow I = \frac{V}{R} = \frac{9}{6} = 1.5A$$

4)

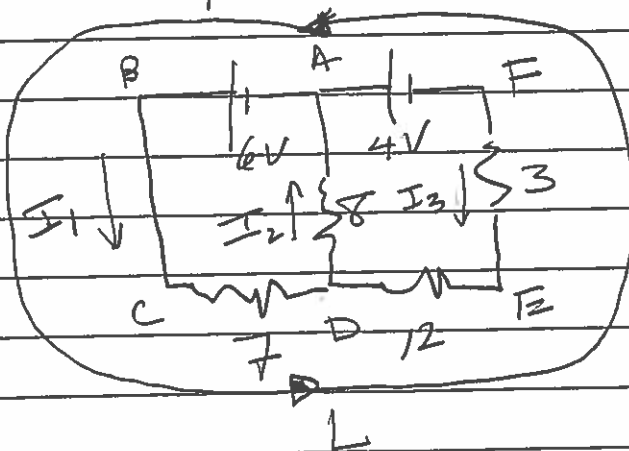

L?

$$6 - 7I_1 + 12I_3 + 3I_3 + 4 = 0$$

$$\Rightarrow 10 - 7I_1 + 15I_3 = 0$$

3

5) E-field  $\rightarrow$  to the left, so a  $-3 \text{ mC}$  charge feels a force to the right regardless of where it is. Thus the statement


"If the charge is placed at D it will move to the left" is wrong

6) Initially  $q_1$   $q_2$  force  $F = 4 \text{ N}$   
 $\leftarrow 5 \text{ m} \rightarrow$   $= \frac{kq_1q_2}{5^2}$

at new separation  $r$ , force is  
 $F' = 100 \text{ N} = \frac{kq_1q_2}{r^2}$

From initial configuration, we know  $kq_1q_2 = 4.25^2 = 100$
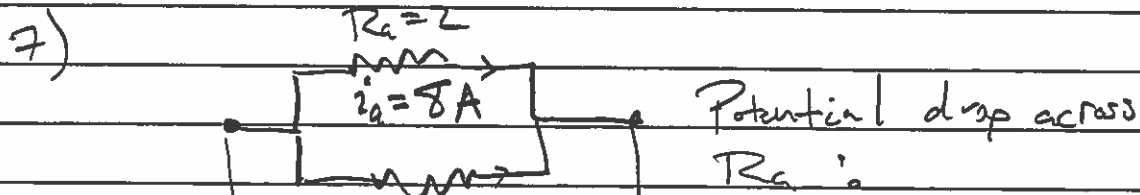
$$\text{So } F' = 100 = \frac{100}{r^2} \Rightarrow r = 1 \text{ m}$$




$$V = i_a R_a = 8 \cdot 2 = 16 \text{ V}$$

$$R_b: i_b = \frac{V}{R_b} = \frac{16 \text{ V}}{4} = 4 \text{ A}$$


since  $V$  is the same across both.

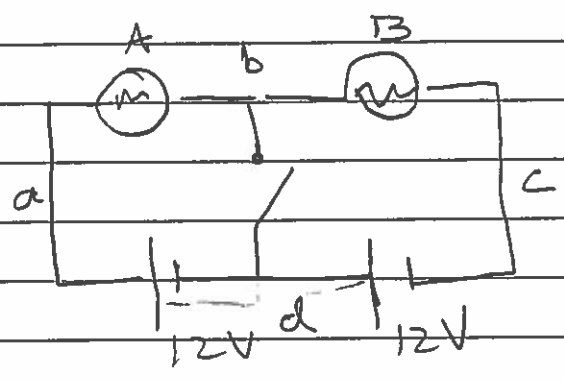8) Since bulbs are identical, the voltage drop across both must be the same, 12V. This means the voltage around the circuit




looks like  $\nabla$

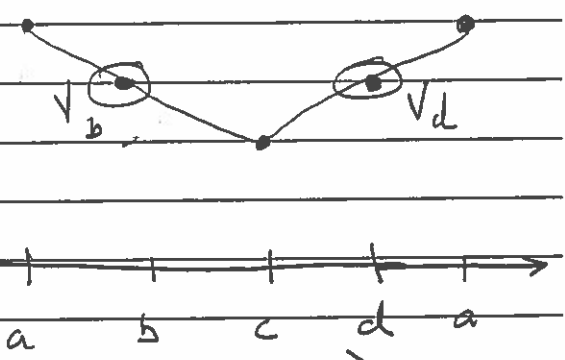$V_b$  and  $V_d$  are the same; therefore closing the switch doesn't lead to any current flow



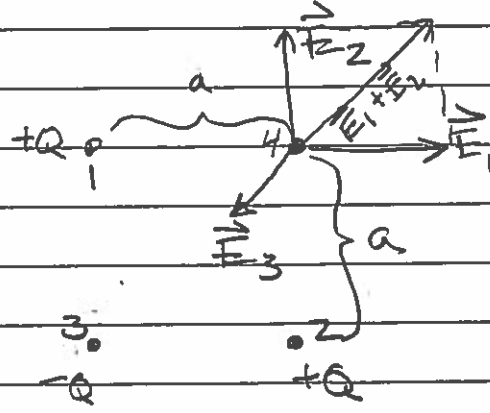9) E-field on charge 4 is the sum of the 3 fields  $\vec{E}_1, \vec{E}_2, \vec{E}_3$



$\vec{E}_1 + \vec{E}_2$  have magnitude  $\frac{kQ}{a^2}$  but they add up to

$|\vec{E}_1 + \vec{E}_2| = \frac{kQ}{a^2} \cdot \sqrt{2}$  up and to right (Pythagorean theorem)  
 They are opposed by  $\vec{E}_3$  with magnitude  $\frac{kQ}{(\sqrt{2}a)^2} = \frac{kQ}{2a^2}$

5

which pts down and to left


$$\vec{E}_1 + \vec{E}_2 \text{ wins since } \frac{kQ}{a^2} \cdot \sqrt{2} > \frac{kQ}{a^2} \cdot \frac{1}{2}$$

So C is correct

10) when spheres touch they share  
 $1.3 \mu\text{C} + (-0.5 \mu\text{C}) = 0.8 \mu\text{C}$  equally  
charge because they are identical,  
So each has  $0.4 \mu\text{C}$ , At 5m separation  
the force is

$$F = \frac{kQ^2}{r^2} = \frac{(9 \times 10^9)(0.4)^2}{5^2}$$
$$= 5.75 \times 10^{-5} \text{ N}$$

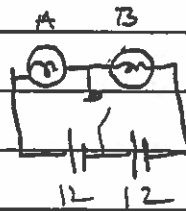11) Total voltage 24V, total  
resistance  $2R$  in series circuit





$$\Rightarrow I = \frac{24}{2R} = \frac{12}{R}$$

$$\text{total power} = \frac{12 \cdot 24}{R} = \frac{2 \cdot 144}{R} = 2 \cdot 14.4$$

$$\Rightarrow R = 10 \Omega$$

6

12)

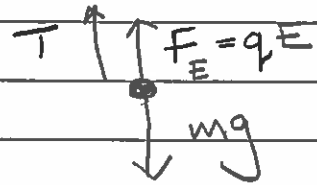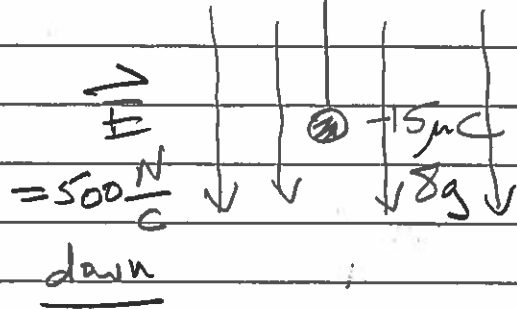

free-body diagram!

T = tension in string  
Forces balance  $\Rightarrow$

$$y\text{-forces: } T + (-15 \mu\text{C})(-500) = (0.008 \text{ kg})(9.8 \frac{\text{m}}{\text{s}^2})$$

$$\Rightarrow T = - (15 \times 10^{-6})(500) + (0.008)(9.8)$$
$$= 7.09 \times 10^{-2} \text{ N}$$